



Trinity College Dublin  
Coláiste na Tríonóide, Baile Átha Cliath  
The University of Dublin

C

## 3C7 DIGITAL SYSTEMS DESIGN LABORATORY


### Lab F

Department of Electronic and Electrical Engineering  
(e-Report submission)



#### Description:

 - A. LFSR Implementation for given LFSR setup (XOR 13-bit)
- B. Advance part (optional implementation)



Submitted by:

**Rohan Taneja**  
**19323238**

**Submission Date: 31/03/2020**

## Part A. LFSR: Implementation

### 1. Task:

Linear Feedback Shift Register implemented is done as explained in Lecture 6. The task was to implement LFSR with feedback as XOR for N=13 bits. Implementation of LFSR required input clock and asynchronous active-high reset.

### 2. Block Diagram:

 


Fig A. (i) – Block diagram made using draw.io

### 3. Testbench:

Simulation takes place under 20 ns clock period and rest high set till 10 cycles. The testbench used is as follows:

```
module lfsr_tb;
    reg clk, reset;
    wire max_tick;
    wire lfsr_out;

    lfsr uut(
        .clk(clk),
        .reset(reset),
        .lfsr_out(lfsr_out),
        .max_tick(max_tick)
    );
    // oscillate clock 20 ns period
    always
    begin
        clk = 1'b1; //high
        #10;
        clk = 1'b0; //low
        #10;
    end

    // reset for first 2 clock cycles
    initial
    begin
        reset = 1'b1;
        #200; // 10 clock cycles high reset
        reset = 1'b0;
    end
endmodule
```

Fig A. (ii) - Testbench for LFSR XOR 13-bit simulation

#### 4. Simulation:

The simulation of my LFSR XOR feedback 13-bit module is as follows.

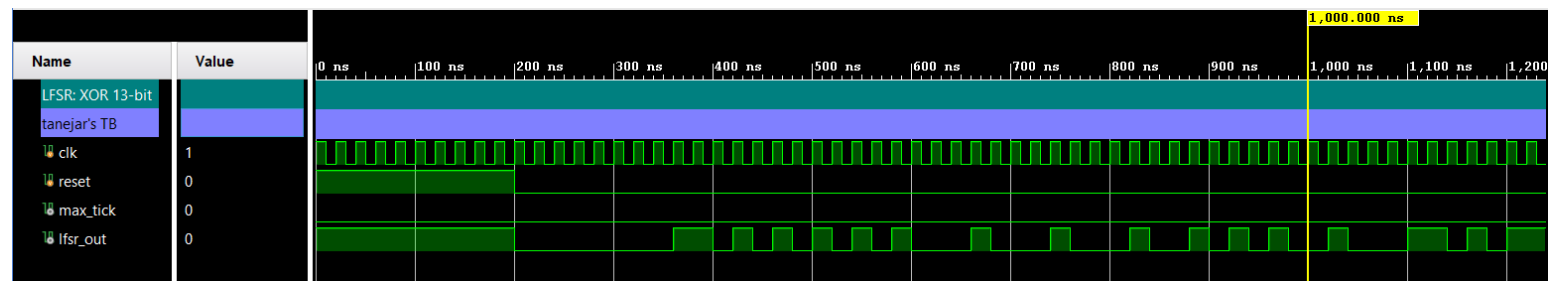


Fig A. (iii) - LFSR simulation for XOR 13-bit – reset after 10<sup>th</sup> cycle

The image below shows that max\_tick signal implementation works well for my 13-bit LFSR implementation as the seed value matches itself after 2<sup>N</sup> - 1 cycles.

 


Fig A. (iv) - LFSR simulation for XOR 13-bit – max\_tick signal after 8201<sup>th</sup> (8191 + 10<sup>th</sup> reset) cycle



Fig A. (v) - LFSR simulation for XOR 13-bit – forbidden seed value – 13'b0000000000000

## 5. Module:

The module LFSR is implemented as follows in Verilog. The local parameter seed value is set in the module. For the forbidden seed value case, value = 13'b0 was used.

```

module lfsr (
    input wire clk, reset,
    output wire [12:0] lfsr_out,
    output reg max_tick
);

    localparam lfsr_seed = 13'b1000000001101; // a seed value

    //signal declaration
    reg [12:0] lfsr_reg; // register storage
    reg [12:0] lfsr_next; // next value
    reg lfsr_tap; // to hold feedback

    integer cycle_ctr; // count the number of lfsr cycles

    always @(posedge clk, posedge reset) // always run on pos clk and reset
        if (reset)
            begin
                lfsr_reg <= lfsr_seed;
                max_tick <= 1'b0; // reset max_tick
                cycle_ctr <= 0; // reset cycle counter
            end
        else
            begin
                lfsr_reg <= lfsr_next;
                cycle_ctr <= cycle_ctr + 1;
                if (cycle_ctr == 2**13 - 1) // max_tick goes high after 2^N -1 cycles
                    max_tick <= 1'b1;
                else
                    max_tick <= 1'b0;
            end

    // next-state logic
    always @*
    begin
        lfsr_tap = lfsr_reg[0] ^ lfsr_reg[2] ^ lfsr_reg[3] ^ lfsr_reg[12];
        // For 13 bit lfsr, generate the feedback by XOR of tap 1st, 3rd, 4th, 13th bits
        // refer from XAPP 052, 1996 issue

        lfsr_next = {lfsr_reg[11:0], lfsr_tap};
        // tap feedback goes at 0 position. other goes shift up
    end

    // output logic
    assign lfsr_out = lfsr_reg[12];

endmodule

```

**Fig A. (vi)** – module lfsr.v – used for the implementation

## Part B. Advanced Implementation

### 1. Task:

To write an extra module which works as counter for MSB (or the feedback tap) generated from LFSR operation and count the number of 0s and 1s feed generated on runtime.

### 2. Schematic:

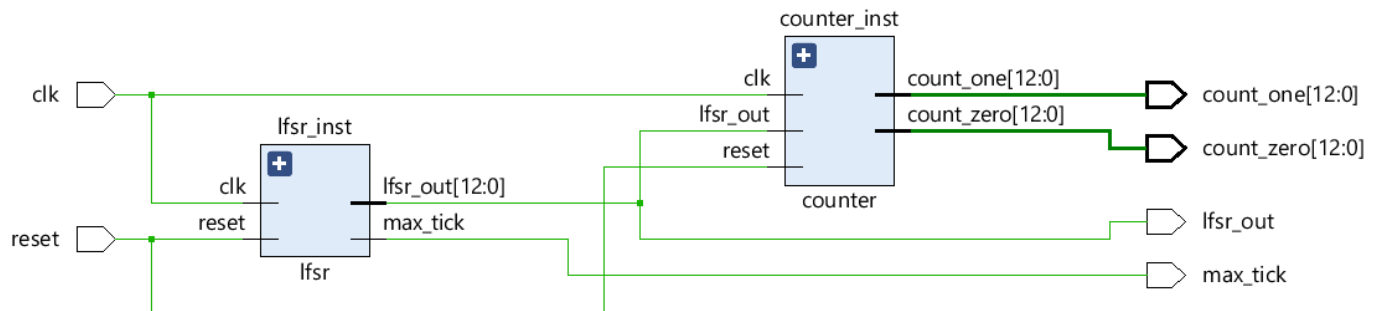


Fig B. (i) – Schematic for Advance Implementation

### 3. Testbench:

Simulation takes place under 20 ns clock period and rest high set till 10 cycles. The testbench used is as follows:

```
module advance_tb;
    reg clk, reset;
    wire max_tick;
    wire lfsr_out;
    wire [12:0] count_zero;
    wire [12:0] count_one;

    advance uut ( // Instantiate the Advance module
        .clk(clk),
        .reset(reset),
        .count_zero(count_zero),
        .count_one(count_one),
        .main_max_tick(max_tick),
        .main_lfsr_out(lfsr_out)
    );

    always
        // oscillate clock 20 ns period
    begin
        clk = 1'b1; //high
        #10;
        clk = 1'b0; //low
        #10;
    end
    initial
    begin
        reset = 1'b1;
        #200; // 10 clock cycles high reset
        reset = 1'b0;
    end
endmodule
```

Fig B. (ii) - Testbench for Advanced part simulation

#### 4. Simulation:

The simulation of my advanced part for LFSR XOR feedback 13-bit module is as follows:

 


Fig B. (iii) – Advanced part – total 0s (0fff) and 1s (1000) counts in full run.

Total 0s counted = 4095

Total 1s counted = 4096

 


Fig B. (iv) – Advanced part – reset counter - max\_tick signal after 8201<sup>th</sup> (8191 + 10<sup>th</sup> reset) cycle

 


Fig B. (v) – Advanced part - the 0s and 1s counter start after reset

 


Fig B. (vi) - LFSR simulation for XOR 13-bit – forbidden seed value – 13'b00000000

## 5. Module:

```

module advance (
    input wire clk, reset,
    output wire [12:0] lfsr_out,
    output reg [12:0] count_one,
    output reg [12:0] count_zero,
    output reg max_tick
);
localparam lfsr_seed = 13'b1000000001101; // a seed value
//signal declaration
reg [12:0] lfsr_reg; // register storage
reg [12:0] lfsr_next; // next value
reg lfsr_tap; // to hold feedback

integer cycle_ctr; // count the number of lfsr cycles

always @(posedge clk, posedge reset) // always run on pos clk and reset
    if (reset)
        begin
            lfsr_reg <= lfsr_seed;
            max_tick <= 1'b0; // reset max_tick
            count_zero <= 13'b0000000000000;
            count_one <= 13'b0000000000000;
            cycle_ctr <= 0; // reset cycle counter
        end
    else
        begin
            lfsr_reg <= lfsr_next;
            cycle_ctr <= cycle_ctr + 1;
            if (cycle_ctr == 2**13 - 1) // max_tick goes high after 2^N -1 cycles
                begin
                    max_tick <= 1'b1;
                    count_zero <= 13'b0000000000000;
                    count_one <= 13'b0000000000000;
                end
            else
                max_tick <= 1'b0;
                begin
                    if (lfsr_out == 1'b1)
                        count_one = count_one + 1;
                    else if (lfsr_out == 1'b0)
                        count_zero = count_zero + 1;
                end
            end
        end

// next-state logic
always @*
begin
    lfsr_tap = lfsr_reg[0] ^ lfsr_reg[2] ^ lfsr_reg[3] ^ lfsr_reg[12];
    // For 13 bit lfsr, generate the feedback by XOR of tap 1st, 3rd, 4th, 13th bits
    // refer from XAPP 052, 1996 issue

    lfsr_next = {lfsr_reg[11:0], lfsr_tap};
    // tap feedback goes at 0 position. other goes shift up
end

// output logic
assign lfsr_out = lfsr_reg[12];

endmodule

```

Fig B. (vii) – module advance.v – used for the implementation

## Comments:

The 0s and 1s generated combined are equal to  $2^N - 1$  cycle. In my case for  $N=13$  bit, we get 8191 cycles out of which 0s were 4095 and 1s were 4096 for the seed value = **b1000000001101**.

## Appendix

The lab F assignment is uploaded along with lfsr.v, lfsr\_tb.v, advance.v and advance\_tb.v. The submission concludes with attached modules and their respective test-benches.

Also, I have attached the test-bench for sequential circuit made for d-flip flop.